

CSE 232 SPRING 2020


PROJECT 2

Murat YILDIZ


1801042004

Note: Multiplication is available only if given a and b inputs positive number, you must enter inputs and press start button to see result, C signal is compare a with 0 and send 1 if $a > 0$, it is enough to press start button 1 cycle.


GENERAL CIRCUIT

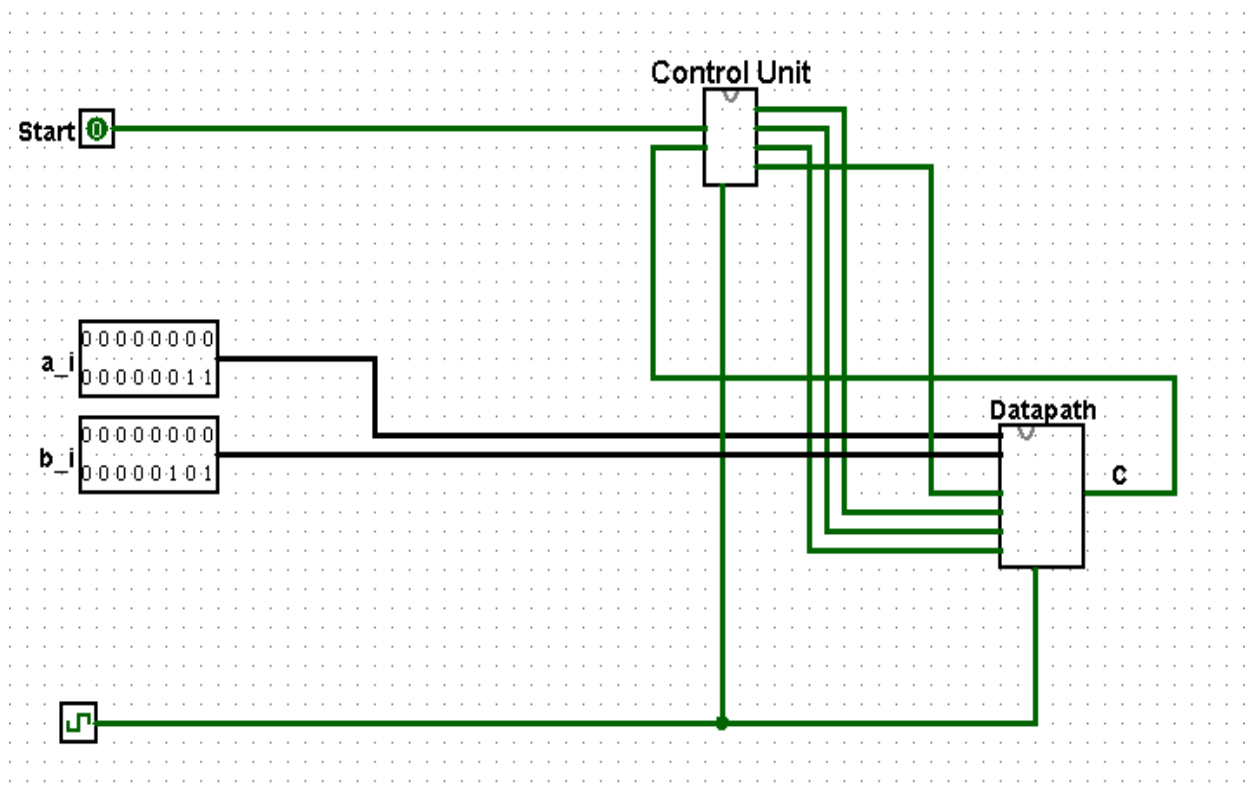

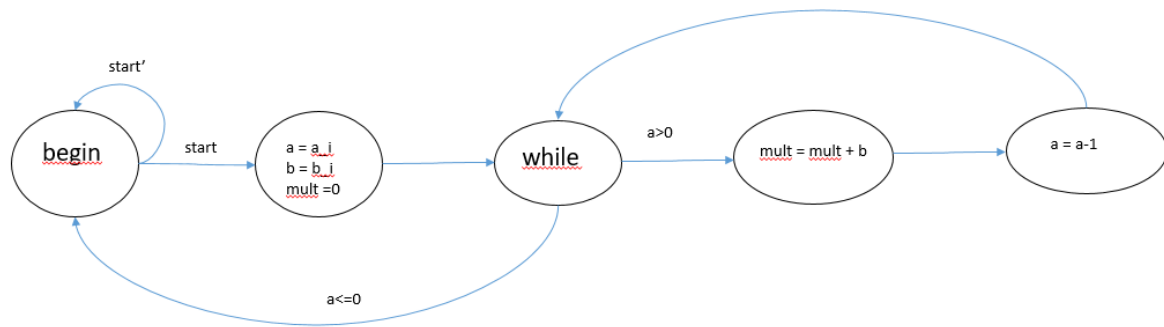
Generalization of C code as state diagram



FSM state diagram

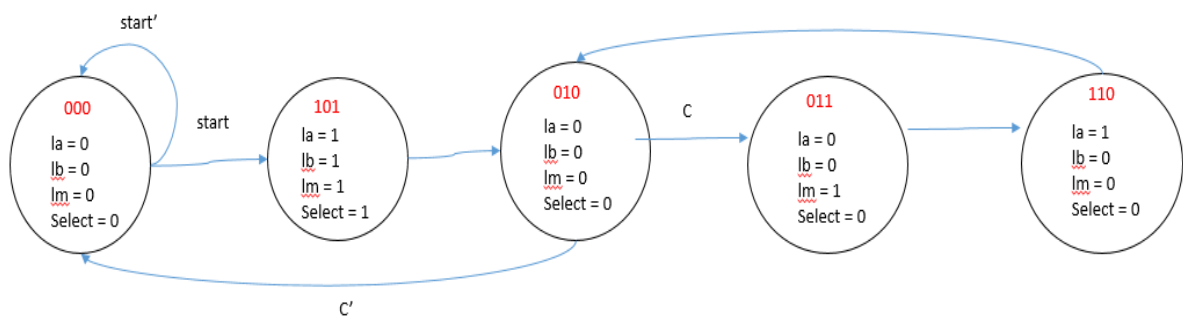

Datapath

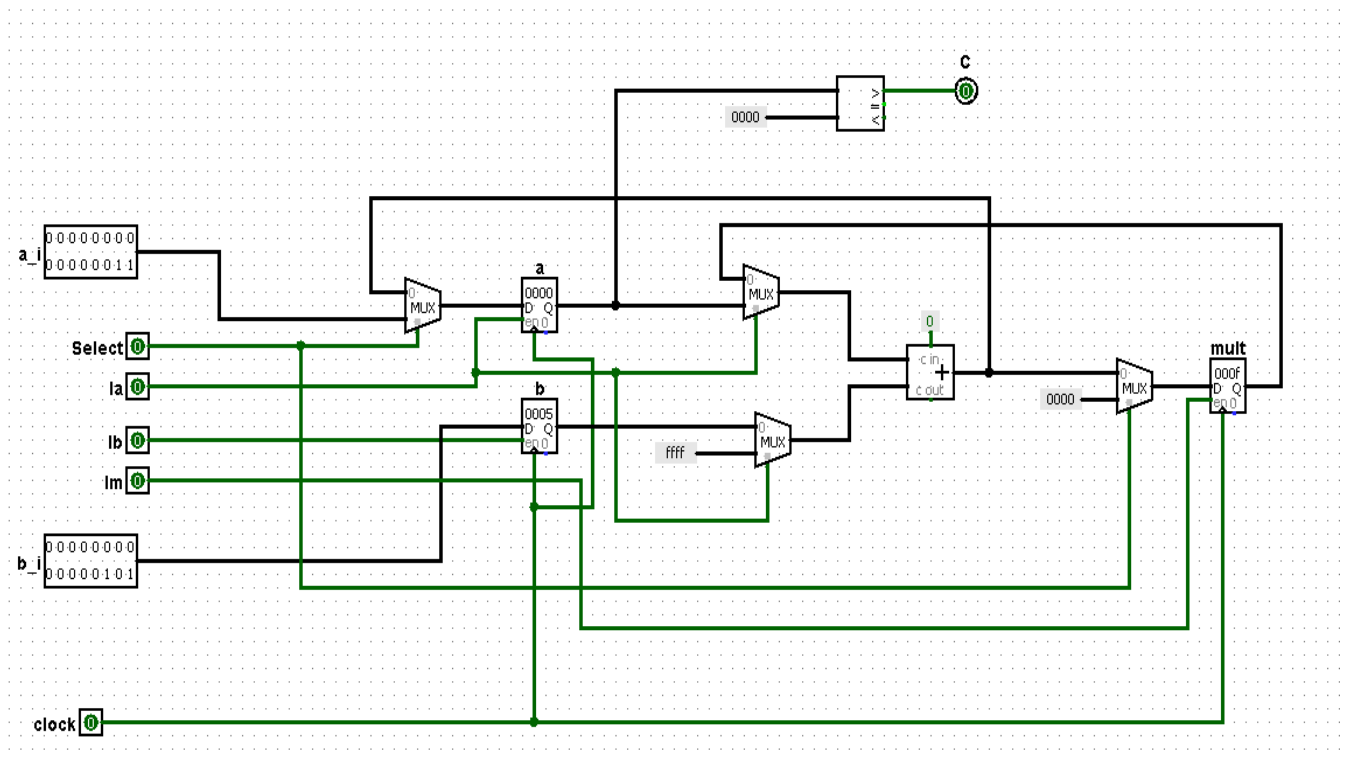

Truth Table

For states

s2	s1	s0	S	C	n2	n1	n0
0	0	0	0	0	0	0	0
0	0	0	0	1	0	0	0
0	0	0	1	0	1	0	1
0	0	0	1	1	1	0	1
0	0	1	0	0	0	0	0
0	0	1	0	1	0	0	0
0	0	1	1	0	0	0	0
0	0	1	1	1	0	0	0
0	1	0	0	0	0	0	0
0	1	0	0	1	0	1	1
0	1	0	1	0	0	0	0
0	1	0	1	1	0	1	1
0	1	1	0	0	1	1	0
0	1	1	0	1	1	1	0
0	1	1	1	0	1	1	0
0	1	1	1	1	1	1	0
1	0	0	0	0	0	0	0
1	0	0	0	1	0	0	0
1	0	0	1	0	0	0	0
1	0	0	1	1	0	0	0
1	0	1	0	0	0	1	0
1	0	1	0	1	0	1	0
1	0	1	1	0	0	1	0
1	0	1	1	1	0	1	0
1	1	0	0	0	0	1	0
1	1	0	0	1	0	1	0
1	1	0	1	0	0	1	0
1	1	0	1	1	0	1	0
1	1	1	0	0	0	0	0
1	1	1	0	1	0	0	0
1	1	1	1	0	0	0	0
1	1	1	1	1	0	0	0

For outputs

s2	s1	s0	la	lb	lm	Select
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	0
0	1	1	0	0	1	0
1	0	0	0	0	0	0
1	0	1	1	1	1	1
1	1	0	1	0	0	0
1	1	1	0	0	0	0

Boolean Expression

For states

$$n2 = \underbrace{s2' s1' s0' S C'}_{(1)} + \underbrace{s2' s1' s0' S C}_{(2)} + \underbrace{s2' s1 s0 S' C'}_{(3)} + \underbrace{s2' s1 s0 S' C}_{(4)} + \underbrace{s2' s1 s0 S C'}_{(5)} + \underbrace{s2' s1 s0 S C}_{(6)}$$

$$= (1-2) s2' s1' s0' S (C' + C) = s2' s1' s0' S 1$$

$$= (3-4-5-6) s2' s1 s0 (S' C' + S' C + S C' + S C) = (S' (C' + C) + S(C' + C)) = (S' + S) = s2' s1 s0 1$$

$$n2 = s2' s1' s0' S + s2' s1 s0$$

$$n1 = \underbrace{s2' s1 s0 S' C'}_{(1)} + \underbrace{s2' s1 s0 S' C}_{(2)} + \underbrace{s2' s1 s0 S C'}_{(3)} + \underbrace{s2' s1 s0 S C}_{(4)} + \underbrace{s2' s1 s0' S' C}_{(5)} + \underbrace{s2' s1 s0' S C}_{(6)}$$

$$+ \underbrace{s2 s1' s0 S' C'}_{(7)} + \underbrace{s2 s1' s0 S' C}_{(8)} + \underbrace{s2 s1' s0 S C'}_{(9)} + \underbrace{s2 s1' s0 S C}_{(10)} + \underbrace{s2 s1 s0' S' C'}_{(11)} + \underbrace{s2 s1 s0' S' C}_{(12)}$$

$$\underbrace{s2 s1 s0' S C'}_{(13)} + \underbrace{s2 s1 s0' S C}_{(14)}$$

$$= (1-2-3-4) s2' s1 s0 (S' C' + S' C + S C' + S C) = (S' (C' + C) + S(C' + C)) = (S' + S) = s2' s1 s0 1$$

$$= (5-6) s2' s1 s0' C (S' + S) = s2' s1 s0' C 1$$

$$= (11-12) s2 s1 s0' C (S' + S) = s2 s1 s0' C 1$$

$$= (\text{result of (5-6)} - \text{result of (11-12)}) s1 s0' C (s2' + s2) = s1 s0' C 1$$

$$= (7-8-9-10) s2 s1' s0 (S' C' + S' C + S C' + S C) = (S' (C' + C) + S(C' + C)) = (S' + S) = s2 s1' s0 1$$

$$= (11-12-13-14) \text{ s2 s1 s0' } (S' C' + S' C + S C' + S C) = (S' (C' + C) + S(C' + C)) = (S' + S) = \text{ s2 s1 s0' } 1$$

$$n1 = s1 s0' C + s2' s1 s0 + s2 s1' s0 + s2 s1 s0'$$

$$n0 = s2' s1' s0' S C' + s2' s1' s0' S C + s2' s1 s0' S' C + s2' s1 s0' S C$$

(1)

(2)

(3)

(4)

$$= (1-2) \text{ s2' s1' s0' S } (C' + C) = \text{ s2' s1' s0' S } 1$$

$$= (3-4) \text{ s2' s1 s0' C } (S' + S) = \text{ s2' s1 s0' C } 1$$

$$n0 = s2' s1' s0' S + s2' s1 s0' C$$

For outputs

$$la = s2 s1' s0 + s2 s1 s0'$$

$$lb = s2 s1' s0$$

$$lm = s2' s1 s0 + s2 s1' s0$$

$$\text{Select} = s2 s1' s0$$

Circuit

